

**Q1. In a series L-C circuit at the resonant frequency the**

- (a) current is maximum (b) current is minimum  
(c) impedance is maximum (d) voltage across C is minimum

**Q2. The time constant of a series R-C circuit is given by**

- (a)  $R/C$  (b)  $RC^2$   
(c)  $RC$  (d)  $R^2C$

**Q3. If resistance is 20  $\Omega$  and inductance is 27 in a R-L series circuit, then time constant of this circuit will be**

- (a) 0.001 s (b) 0.1 s  
(c) 10 s (d) 100 s

**Q4. Which of the following coil will have large resonant frequency?**

- (a) A coil with large resistance (b) A coil with low resistance  
(c) A coil with large distributed capacitance (d) A coil with low distributed capacitance

**Q5. If a sinusoidal wave has frequency of 50 Hz with 30 A r.m.s. current which of the following equation represents this wave?**

- (a)  $42.42 \sin 314t$  (b)  $60 \sin 25t$   
(c)  $30 \sin 50t$  (d)  $84.84 \sin 25t$

**Q6. The safest value of current the human body can carry for more than 3 second is**

- (a) 4 mA (b) 9 mA  
(c) 15 mA (d) 25 mA

**Q7. A pure inductance connected across 250 V, 50 Hz supply consumes 100 W. This consumption can be attributed to**


- (a) the big size of the inductor (b) the reactance of the inductor  
(c) the current flowing in the inductor (d) the statement given is false

**Q8. The input of an A.C. circuit having power factor of 0.8 lagging is 40 kVA The power drawn by the circuit is**

- (a) 12 kW (b) 22 kW  
(c) 32 kW (d) 64 kW

**Q9. The effective resistance of an iron-cored choke working on ordinary supply frequency is more than its true resistance because of**

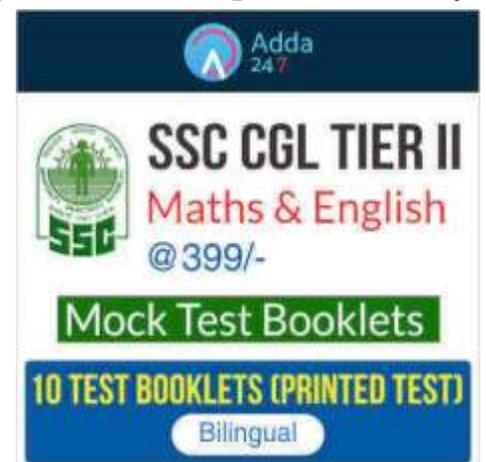- (a) iron loss in core  
(b) skin effect  
(c) increase in temperature  
(d) capacitive effect between adjacent coil turns



Advertisement for Adda247 Mock Test Booklets for SSC CGL Tier II Maths & English. The ad features the Adda247 logo at the top, followed by the text "SSC CGL TIER II Maths & English @399/-". Below this, it says "Mock Test Booklets" and "10 TEST BOOKLETS (PRINTED TEST)". At the bottom, it indicates "Bilingual".

**Q10. In an AC. circuit, a low value of kVAR compared with kW indicates**

- (a) low efficiency
- (b) high power factor
- (c) unity power factor
- (d) maximum load current

**Q11. In AC. circuits, laminated iron is invariably used in order to**

- (a) reduce eddy current loss
- (b) increase heat radiation
- (c) make assembly cheap and easier
- (d) reduce circuit permeability

**Q12. The ratio of active power to apparent power is known as factor.**

- (a) demand
- (b) load
- (c) power
- (d) form

**Q13. All definitions of power factor of a series R-L-C circuit are correct except**

- (a) ratio of net reactance and impedance
- (b) ratio of kW and kVA
- (c) ratio of J and Z
- (d) ratio of W and VA

**Q14. The apparent power drawn by an A.C. circuit is 10 kVA and active power is 8 kW. The reactive power in the circuit is**

- (a) 4 kVAR
- (b) 6 kVAR
- (c) 8 kVAR
- (d) 16 kVAR

**Q15. What will be the phase angle between two alternating waves of equal frequency, when one wave attains maximum value the other is at zero value ?**

- (a)  $0^\circ$
- (b)  $45^\circ$
- (c)  $90^\circ$
- (d)  $180^\circ$

**Q16. The purpose of a parallel circuit resonance is to magnify**

- (a) current
- (b) voltage
- (c) power
- (d) frequency

**Q17. In an A.C. circuit power is dissipated in**

- (a) resistance only
- (b) inductance only
- (c) capacitance only
- (d) none of the above

**Q18. In a parallel R-C circuit, the current always\_\_\_\_\_the applied voltage**

- (a) lags
- (b) leads
- (c) remains in phase with
- (d) none of the above

**Q19. At very low frequencies a series R-C circuit behaves as almost purely**

- (a) resistive
- (b) inductive
- (c) capacitive
- (d) none of the above

**Q20. Skin effect occurs when a conductor carries current at\_\_\_\_\_ frequencies.**

- (a) very low
- (b) low
- (c) medium
- (d) high

**Q21. At \_\_\_\_\_ frequencies the parallel R-L circuit behaves as purely resistive.**

- (a) low
- (b) very low
- (c) high
- (d) very high

**Q22. In a sine wave the slope is constant**

- (a) between  $0^\circ$  and  $90^\circ$
- (b) between  $90^\circ$  and  $180^\circ$
- (c) between  $180^\circ$  and  $270^\circ$
- (d) no where

**Q23. The power is measured in terms of decibels in case of**

- (a) electronic equipment
- (b) transformers
- (c) current transformers
- (d) auto transformers

**Q24. Capacitive susceptance is a measure of**

- (a) reactive power in a circuit
- (b) the extent of neutralisation of reactive power in a circuit
- (c) a purely capacitive circuit's ability to pass current
- (d) a purely capacitive circuit's ability to resist the flow of current

**Q25. Which of the following statements pertains to resistors only?**

- (a) can dissipate considerable amount of power
- (b) can act as energy storage devices
- (c) connecting them in parallel increases the total value
- (d) oppose sudden changes in voltage

**Q26. Which of the following refers to a parallel circuit ?**

- (a) The current through each element is same
- (b) The voltage across element is in proportion to it's resistance value
- (c) The equivalent resistance is greater than any one of the resistors
- (d) The current through any one element is less than the source current

**Q27. Aphasoris**

- (a) a line which represents the magnitude and phase of an alternating quantity
- (b) a line representing the magnitude and direction of an alternating quantity
- (c) a coloured tag or band for distinction between different phases of a 3-phase supply
- (d) an instrument used for measuring phases of an unbalanced 3-phase load

**Q28. A parallel AC. circuit in resonance will**

- (a) have a high voltage developed across each inductive and capacitive section
- (b) have a high impedance
- (c) act like a resistor of low value
- (d) have current in each section equal to the line current

**CAREER POWER**  
AN IIT/IIM ALUMNI COMPANY

**SSC CGL 2017**  
All Rounder

**350+ TOTAL TEST**

- 80+ TIER-I MOCKS
- 50+ TIER-II MOCKS
- 200+ SECTIONAL TEST

Bilingual

**Q29. Wire-wound resistors are unsuitable for use at high frequencies because they**

- (a) create more electrical noise
- (b) are likely to melt under excessive eddy current heat
- (c) consume more power
- (d) exhibit unwanted inductive and capacitive effects

**Q30. The inductance of a coil can be increased by**

- (a) increasing core length
- (b) decreasing the number of turns
- (c) decreasing the diameter of the former
- (d) choosing core material having high relative permeability

**Q31. Which of the following waves has the highest value of peak factor ?**

- (a) Square wave
- (b) Sine wave
- (c) Half wave rectified sine wave
- (d) Triangular wave

**Q32. The frequency of domestic power supply in India is**

- (a) 200 Hz
- (b) 100 Hz
- (c) 60 Hz
- (d) 50 Hz

**Q33. The r.m.s. value of half wave rectified sine wave is 200 V. The r.m.s. value of full wave rectified AC. will be**

- (a) 282.8 V
- (b) 141.4 V
- (c) 111 V
- (d) 100 V

**Q34. The r.m.s. value of pure cosine function is**

- (a) 0.5 of peak value
- (b) 0.707 of peak value
- (c) same as peak value
- (d) zero

**Q35. Ohm is unit of all of the following except**

- (a) inductive reactance
- (b) capacitive reactance
- (c) resistance
- (d) capacitance

**Q36. The series and parallel resonance on L-C circuit' differs in that**

- (a) series resonance needs a low-resistance source for sharp rise in current
- (b) series resonance needs a high-resistance source for sharp increase in current
- (c) parallel resonance needs a low-resistance source for a sharp increase in impedance
- (d) parallel resonance needs a low-resistance source for a sharp rise in line current

**Q37. The phasors for which of the following pair are 180° out of phase for VL, VC and VR?**

- (a) Vc and VR
- (b) VL and VR
- (c) Vc and VL
- (d) none of the above

**Q38. The frequency of an alternating current is**

- (a) the speed with which the alternator runs
- (b) the number of cycles generated in one minute
- (c) the number of waves passing through a point in one second
- (d) the number of electrons passing through a point in one second

**Q39. A pure capacitor connected across an A.C. voltage consumed 50 W. This is due to**

- (a) the capacitive reactance in ohms
- (b) the current flowing in capacitor
- (c) the size of the capacitor being quite big
- (d) the statement is incorrect

**Q40. The power factor of a D.C. circuit is always**

- (a) less than unity
- (b) unity
- (c) greater than unity
- (d) zero

**Q41. The product of apparent power and cosine of the phase angle between circuit voltage and current is**

- (a) true power
- (b) reactive power
- (c) volt-amperes
- (d) instantaneous power

**Q42. The equation of 50 Hz current sine wave having r.m.s. value of 60 A is**

- (a)  $60 \sin 25 t$
- (b)  $60 \sin 50 t$
- (c)  $84.84 \sin 314 t$
- (d)  $42.42 \sin 314 t$

**Q43. An A.C. voltage is impressed across a pure resistance of 3.5 ohms in parallel with a pure inductance of impedance of 3.5 ohms,**

- (a) the current through the resistance is more
- (b) the current through the resistance is less
- (c) both resistance and inductance carry equal currents
- (d) none of the above

**Q44. In a pure inductive circuit if the supply frequency is reduced to  $1/2$ , the current will**

- (a) be reduced by half
- (b) be doubled
- (c) be four times as high
- (d) be reduced to one fourth

**Q45. In a pure capacitive circuit if the supply frequency is reduced to  $1/2$ , the current will**

- (a) be reduced by half
- (b) be doubled
- (c) be four times at high
- (d) be reduced to one fourth



**CAREER POWER**  
AN IIT/IIM ALUMNI COMPANY



**SSC CGL 2017**  
TIER-II & TIER-III  
All Rounder

**100+ TOTAL TEST**

- 60 Full Length Mocks
- 50 Topicwise (Advance Maths)
- 20 eBooks (Topic Wise)
- English Descriptive eBook

**Q46. When an alternating current passes through an ohmic resistance the electrical power converted into heat is**

- (a) apparent power
- (b) true power
- (c) reactive power
- (d) none of the above

**Q47. In each of the three coils of a three phase generator, an alternating voltage having an r.m.s. value of 220 V is induced. Which of the following values is indicated by the voltmeters ?**

- (a) 220 V
- (b)  $220\sqrt{3}$  V
- (c)  $220/\sqrt{3}$  V
- (d) none of the above

**Q48. A 8-bit serial in / parallel out shift register contains the value "8", \_\_\_\_\_ clock signal(s) will be required to shift the value completely out of the register.**

- (a) 1
- (b) 2
- (c) 4
- (d) 8

**Q49. In a sequential circuit the next state is determined by \_\_\_\_\_ and \_\_\_\_\_.**

- (a) State variable, current state
- (b) Current state, flip-flop output
- (c) Current state and external input
- (d) Input and clock signal applied

**Q50. The divide-by-60 counter in digital clock is implemented by using two cascading counters:**

- (a) Mod-6, Mod-10
- (b) Mod-50, Mod-10
- (c) Mod-10, Mod-50
- (d) Mod-50, Mod-6

**Q51. The sensitivity of human eyes is maximum at**

- (a) white portion of spectrum
- (b) green portion of spectrum
- (c) red portion of spectrum
- (d) violet portion of spectrum

**Q52. In a bipolar transistor, the base collector junction has**

- (a) forward bias
- (b) reverse bias
- (c) zero bias
- (d) zero or forward bias

**Q53. An intrinsic silicon sample has 1 million free electrons at room temperature. As the temperature is increased**

- (a) the number of free electrons increases
- (b) the number of free electrons increases but the number of holes decreases
- (c) the number of free electrons and holes increase by the same amount
- (d) the number of free electrons and holes increase but not by the same amount

**Q54. What is the necessary a.c. input power from the transformer secondary used in a half wave rectifier to deliver 500 W of d.c. power to the load?**

- (a) 1232 W
- (b) 848 W
- (c) 616 W
- (d) 308 W

**Q55. In a semi-conductor diode, the barrier offers opposition to**

- (a) holes in P-region only
- (b) free electrons in N-region only
- (c) majority carriers in both regions
- (d) majority as well as minority carriers in both regions

**Q56. In a half wave rectifier, the load current flows**

- (a) only for the positive half cycle of the input signal
- (b) only for the negative half cycle of the input signal
- (c) for full cycle
- (d) for less than fourth cycle

**Q57. For a NPN bipolar transistor, what is the main stream of current in the base region?**

- (a) Drift of holes
- (b) Diffusion of holes
- (c) Drift of electrons
- (d) Diffusion of electrons

**Q58. Assertion (A):** A VMOS can handle much larger current than other field effect transistors.

**Reason (R):** In a VMOS the conducting channel is very narrow.

- (a) Both A and R are true and R is correct explanation of A
- (b) Both A and R are true but R is not a correct explanation of A
- (c) A is true but R is false
- (d) A is false but R is true

**Q59. In monolithic ICs, all the components are fabricated by**

- (a) diffusion process
- (b) oxidation
- (c) evaporation
- (d) none

**Q60. Which one of the following is not a characteristic of a ferroelectric material?**

- (a) High dielectric constant
- (b) No hysteresis
- (c) Ferroelectric characteristic only above the curie point
- (d) Electric dipole moment

**Q61. In the sale of diamonds the unit of weight is carat. One carat is equal to**

- (a) 100 mg
- (b) 150 mg
- (c) 200 mg
- (d) 500 mg

**Q62. Assertion (A):** A JFET can be used as a current source.

**Reason (R):** In beyond pinch off region the current in JFET is nearly constant.

- (a) Both A and R are true and R is correct explanation of A
- (b) Both A and R are true but R is not a correct explanation of A
- (c) A is true but R is false
- (d) A is false but R is true

**Q63. Permalloy is**

- (a) a variety of stainless steel
- (b) a polymer
- (c) a conon-ferrous alloy used in aircraft industry
- (d) a nickel an iron alloy having high permeability

**CAREER POWER**  
AN IIT/IIM ALUMNI COMPANY

**SSC 2017**  
(COMPLETE KIT)

**400+ TOTAL TEST**

- 200+ MOCKS
- 200+ SECTIONAL TEST

Bilingual

**Q64. Which of the following could be the maximum current rating of junction diode by 126?**

- (a) 1 A
- (b) 10 A
- (c) 20 A
- (d) 100 A

**Q65. Each cell of a static Random Access memory contains**

- (a) 6 MOS transistor
- (b) 4 MOS transistor, 2 capacitor
- (c) 2 MOS transistor, 4 capacitor
- (d) 1 MOS transistor and 1 capacitor

**Q66. An electron in the conduction band**

- (a) has higher energy than the electron in the valence band
- (b) has lower energy than the electron in the valence band
- (c) loses its charge easily
- (d) jumps to the top of the crystal

**Q67. The dynamic resistance of a forward biased p-n diode**

- (a) varies inversely with current
- (b) varies directly with current
- (c) is constant
- (d) is either constant or varies directly with current

**Q68. A thermistor is a**

- (a) thermocouple
- (b) thermometer
- (c) miniature resistance
- (d) heat sensitive explosive

**Q69. When diodes are connected in series to increase voltage rating the peak inverse voltage per junction**

- (a) should not exceed half the breakdown voltage
- (b) should not exceed the breakdown voltage
- (c) should not exceed one third the breakdown voltage
- (d) may be equal to or less than breakdown voltage

**Q70. Hall effect is observed in a specimen when it is carrying current and is placed in a magnetic field. The resultant electric field inside the specimen is**

- (a) normal to both current and magnetic field
- (b) in the direction of current
- (c) antiparallel to magnetic field
- (d) in arbitrary direction

**Q71. In an ideal diode there is no breakdown, no \_\_\_\_\_ current, and no forward \_\_\_\_\_ drop.**

- (a) reverse, voltage
- (b) forward, current
- (c) forward, voltage
- (d) reverse, current

**Q72. Silicon is not suitable for fabrication of light emitting diodes because it is**

- (a) an indirect band gap semiconductor
- (b) direct band gap semiconductor
- (c) wideband gap semiconductor
- (d) narrowband gap semiconductor

**Q73. MOSFET can be used as a**

- (a) current controlled capacitor
- (b) voltage controlled capacitor
- (c) current controlled inductor
- (d) voltage controlled inductor

**Q74. Power diodes are generally**

- (a) silicon diodes
- (b) germanium diodes
- (c) either of the above
- (d) none of the above

**Q75. The depletion layer width of Junction**

- (a) decreases with light doping
- (b) is independent of applied voltage
- (c) is increased under reverse bias
- (d) increases with heavy doping

**Q76. Forbidden energy gap in germanium at 0 K is about**

- (a) 10 eV
- (b) 5 eV
- (c) 2 eV
- (d) 0.78 eV

**Q77. Light dependent resistors are**

- (a) highly doped semiconductor
- (b) intrinsic semiconductor
- (c) lightly doped semiconductor
- (d) either (a) or (c)

**Q78. Fermi level is the amount of energy in which**

- (a) a hole can have at room temperature
- (b) an electron can have at room temperature
- (c) must be given to an electron move to conduction band
- (d) none of the above

**Q79. An ideal Op-amp is an ideal**

- (a) voltage controlled current source
- (b) voltage controlled voltage source
- (c) current controlled current source
- (d) current controlled voltage source

**Q80. Free electrons exist in**

- (a) first band
- (b) second band
- (c) third band
- (d) conduction band

**Q81. In an ideal diode there is no breakdown, no \_\_\_\_\_ current, and no forward \_\_\_\_\_ drop.**

- (a) reverse, voltage
- (b) forward, current
- (c) forward, voltage
- (d) reverse, current

**Q82. Silicon is not suitable for fabrication of light emitting diodes because it is**

- (a) an indirect band gap semiconductor
- (b) direct band gap semiconductor
- (c) wideband gap semiconductor
- (d) narrowband gap semiconductor

**Q83. MOSFET can be used as a**

- (a) current controlled capacitor
- (b) voltage controlled capacitor
- (c) current controlled inductor
- (d) voltage controlled inductor



**Q84. Power diodes are generally**

- (a) silicon diodes
- (b) germanium diodes
- (c) either of the above
- (d) none of the above

**Q85. The depletion layer width of Junction**

- (a) decreases with light doping
- (b) is independent of applied voltage
- (c) is increased under reverse bias
- (d) increases with heavy doping

**Q86. Forbidden energy gap in germanium at 0 K is about**

- (a) 10 eV
- (b) 5 eV
- (c) 2 eV
- (d) 0.78 eV

**Q87. Light dependent resistors are**

- (a) highly doped semiconductor
- (b) intrinsic semiconductor
- (c) lightly doped semiconductor
- (d) either (a) or (c)

**Q88. Fermi level is the amount of energy in which**

- (a) a hole can have at room temperature
- (b) an electron can have at room temperature
- (c) must be given to an electron move to conduction band
- (d) none of the above

**Q89. An ideal Op-amp is an ideal**

- (a) voltage controlled current source
- (b) voltage controlled voltage source
- (c) current controlled current source
- (d) current controlled voltage source

**Q90. Free electrons exist in**

- (a) first band
- (b) second band
- (c) third band
- (d) conduction band

**Q91. As compared to bipolar junction transistor, a FET**

- (a) is less noisy
- (b) has better thermal stability
- (c) has higher input resistance
- (d) all of the above

**Q92. For a P-N diode, the number of minority carriers crossing the junction depends on**

- (a) forward bias voltage
- (b) potential barrier
- (c) rate of thermal generation of electron hole pairs
- (d) none of the above

**Q93. Which variety of copper has the best conductivity?**

- (a) Pure annealed copper
- (b) Hard drawn copper
- (c) Induction hardened copper
- (d) Copper containing traces of silicon

**Q94. The output, V-I characteristics of an Enhancement type MOSFET has**

- (a) only an ohmic region
- (b) only a saturation region
- (c) an ohmic region at low voltage value followed by a saturation region at higher voltages
- (d) an ohmic region at large voltage values preceded by a saturation region at lower voltages

**Q95. Piezoelectric quartz crystal resonators find application where**

- (a) signal amplification is required
- (b) rectification of the signal is required
- (c) signal frequency control is required
- (d) modulation of signal is required

**Q96. The forbidden energy gap between the valence band and conduction band will be least in case of**

- (a) metals
- (b) semiconductors
- (c) insulators
- (d) all of the above

**Q97. If too large current passes through the diode**

- (a) all electrons will leave
- (b) all holes will freeze
- (c) excessive heat may damage the diode
- (d) diode will emit light

**Q98. In a bipolar transistor, the emitter base junction has**

- (a) forward bias
- (b) reverse bias
- (c) zero bias
- (d) zero or reverse bias

**Q99. A sine wave has a frequency of 50 Hz. Its angular frequency is \_\_\_\_\_ radian/second.**

- (a) 100 n
- (b) 50 jt
- (c) 25 JT
- (d) 5 n

**Q100. The reactance offered by a capacitor to alternating current of frequency 50 Hz is 20 Q. If frequency is increased to 100 Hz, reactance becomes \_\_\_\_ ohms.**

- (a) 2.5
- (b) 5
- (c) 10
- (d) 15

**CAREER POWER**  
AN IIT/IIM ALUMNI COMPANY

**SSC CPO 2017**  
TIER-II

**TOTAL VACANCIES-2355**

**10 MOCKS**